

Challenges in Low-Power Analog Circuit Design for sub-28nm CMOS Technologies

Amr Fahim


Semtech Corporation

Outline

- **Scaling Effects**
- **Design Methodology**
- **Challenges in sub-28nm CMOS**
- **Analog Design for sub-28nm CMOS**
- **Design Examples**
- **Conclusions**

Scaling Effects

- Transistor cross section:

 

$$V_s = \frac{C_{ox} \cdot V_g + C_d \cdot V_d}{C_{ox} \left(1 + \frac{C_d}{C_{ox}}\right) + C_{dep}} \rightarrow V_s \propto V_d$$

$$V_b = \frac{C_{oxe} \cdot V_g + C_d \cdot V_d}{C_{oxe} \left(1 + \frac{C_d}{C_{ox}}\right) + C_{dep}}$$


→ $I_{leakage}$ more in deep substrate

Where: $C_{oxe} = \frac{C_{ox} \cdot C_{dep1}}{C_{ox} + C_{dep1}}$

- Known as *drain induced barrier lowering* (DIBL)
- As L scales: 1) $C_{ox} \uparrow$ 2) $W_{dep} \downarrow$ (body doping)

Scaling Effects



- Leakage current scaling (W=1um)

 

$$I_D = I_{S0} W e^{\frac{q}{KT}} (A V_{GS} + B V_{DS})$$

Scaling Effects

 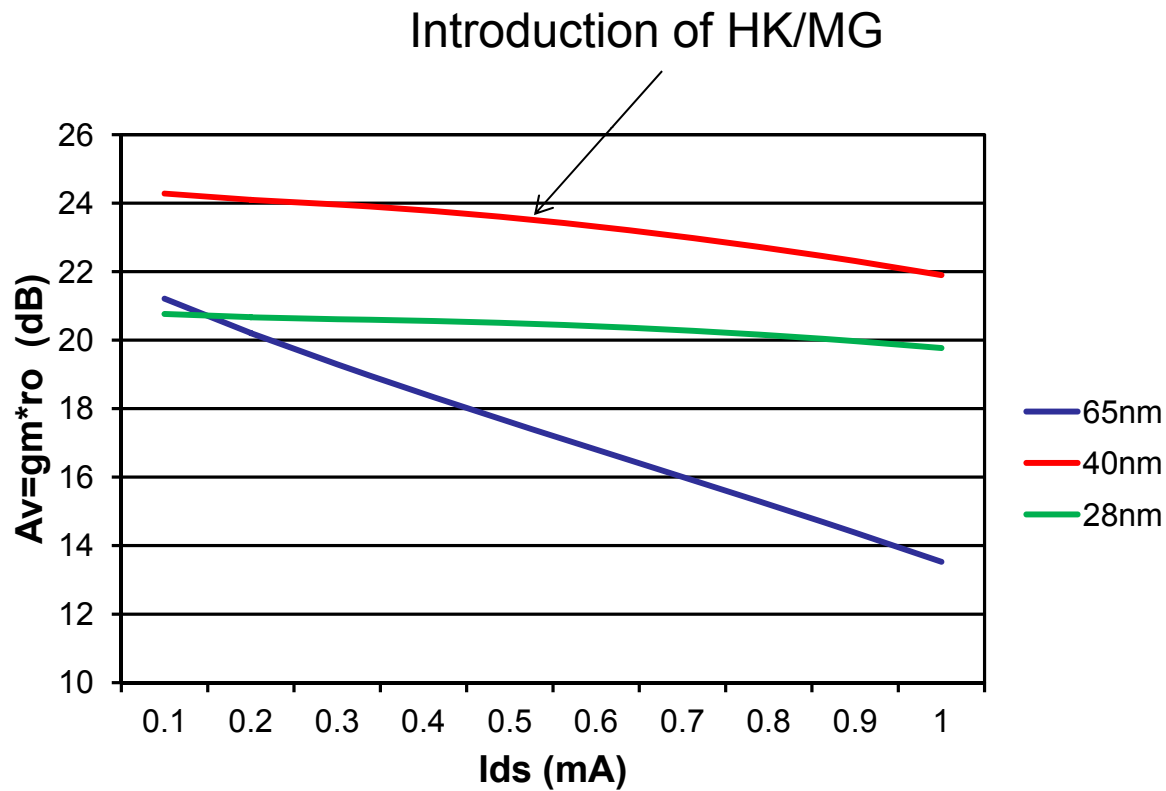- Intrinsic Transistor Gain: $A_v = g_m \cdot r_o$




Outline

- Scaling Effects
- **Design Methodology**
- Challenges in sub-28nm CMOS
- Analog Design for Sub-28nm CMOS
- Design Examples
- Conclusions


Design Methodology

 - Important Figure-of-merit in analog design is the G_m/I_{DS} ratio



Design Methodology

 - Other important metrics in analog design include:
 - Noise: limits the minimum detectable signal (MDS) that the analog circuit can process
 - Linearity: limits the maximum possible signal that the analog circuit can process



- Noise+Linearity \rightarrow define the “dynamic range” (DR) of the signal that the circuit can handle

$$DR = \frac{2}{3}(IIP3 - MDS)$$

Design Methodology

- Other important metrics in analog design include:
 - Gain (g_m), Bandwidth (F_t), power consumption
- Define a “figure-of-merit” (FOM) to take into account dynamic range and bandwidth
 - This FOM describes maximum performance without regard to power consumption


$$FOM = 10 \log(f_T) + \frac{2}{3} \left(IIP3 - 10 \log \left(\int v_n^2 df \right) \right)$$

Bandwidth

Dynamic range

Design Methodology

- FOM plot over current consumption:

 

$$FOM = 10 \log(f_T) + \frac{2}{3} \left(IIP3 - 10 \log \left(\int v_n^2 df \right) \right)$$

Design Methodology

- Define another “figure-of-merit” (FOM2) to take into account current consumption as well
 - FOM2 takes into account the current efficiency in obtaining a certain performance level

$$FOM2 = 10 \log \left(\frac{g_m}{I_{ds}} \right) + 10 \log (f_T) + \frac{2}{3} \left(IIP3 - 10 \log \left(\int v_n^2 df \right) \right)$$


Power
Efficiency

Bandwidth

Dynamic
Range

Design Methodology

- FOM2 plot over current consumption

 

$$FOM2 = 10 \log \left(\frac{g_m}{I_{ds}} \right) + 10 \log(f_T) + \frac{2}{3} \left(IIP3 - 10 \log \left(\int v_n^2 df \right) \right)$$

Design Methodology

- Overall design methodology:
 1. Generate parametric curves based on FOM or FOM2 (I_{ds} and W are parameters)
 2. Choose I_{ds} and W that meet desired specifications

Outline

- Scaling Effects
- Design Methodology
- **Challenges in sub-28nm CMOS**
- Analog Design for Sub-28nm CMOS
- Design Examples
- Conclusions



Challenges in sub-28nm CMOS

- **Stress effects (isolation proximity):**

- **Stress = Force / Area**

- **Stress scenarios:**

1. **Force = $q * E$**

  


Devices near interface experience "stress"

2. **Stress is also induced by interface boundaries between material with different dopant densities (adjacent NFETs or NFET/PFET boundary)**

- **Effect of stress → carrier mobility shifts (current!)**
- **Mitigate by use of dummies & equally spaced devices**


Challenges in sub-28nm CMOS

 - Diffusion proximity (well proximity)
 - Dopant atoms scattered from adjacent photoresist



- Mitigate by use of dummies

 
Scattering → variability in doping profile
VT variation in order to 10's mV



Source: Freescale Semiconductor (0.13um 3.3V NFET)

Challenges in sub-28nm CMOS

 - Device gate leakage:
 - Gate leakage caused by quantum tunneling effect




$$i_{GS} \approx C_{ox} \cdot W \cdot L \cdot f_{gate}$$


Introduction of HK/MG

Challenges in sub-28nm CMOS

 - Gate leakage introduce low-frequency pole:



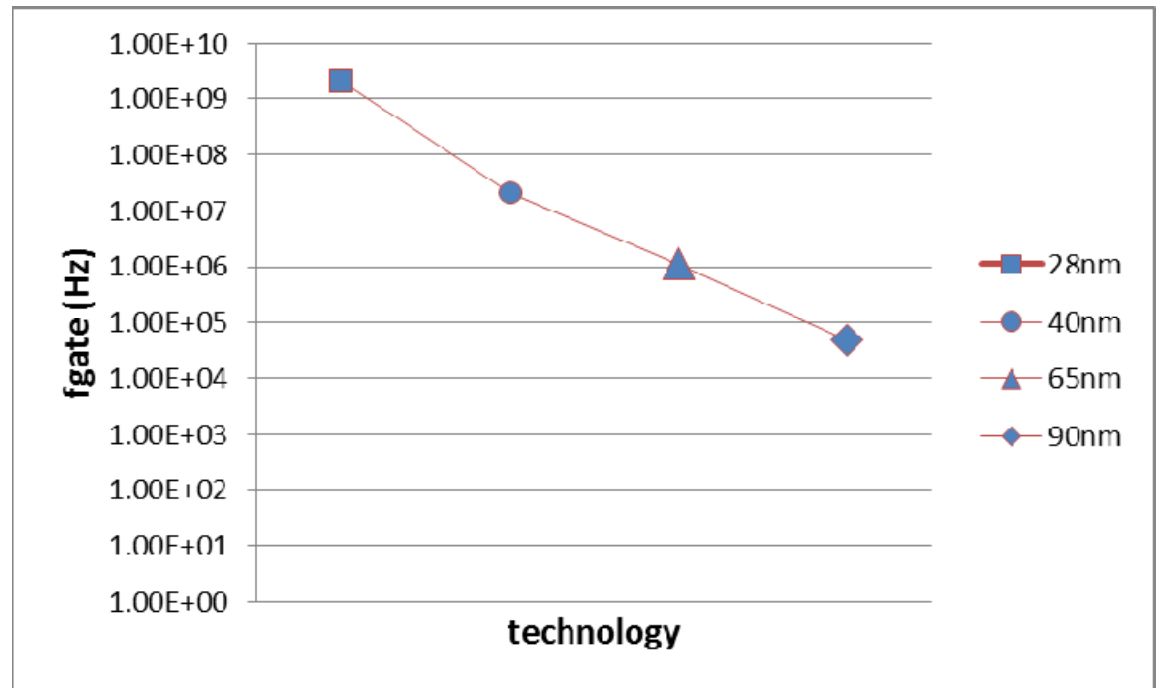
$$f_{gate} = \frac{g_{tunnel}}{2\pi C_{in}}$$



- This creates a low-frequency bound on sample-and-hold (S/H) circuits as well as low-frequency RC filters (such as PLL loop filters)

Challenges in sub-28nm CMOS

 - Gate leakage causes mismatch in current mirrors:



Gate leakage causes current mismatch

Classical mismatch:

$$\left(\frac{\Delta I}{I}\right)^2 = \left(\frac{A_{VT}}{\sqrt{WL}} \cdot \frac{g_m}{I}\right)^2$$

Mismatch with gate tunneling:


$$\left(\frac{\Delta I}{I}\right)^2 = \left(\frac{A_{VT}}{\sqrt{WL}} \cdot \frac{g_m}{I}\right)^2 + \left(\frac{X_{IGS}}{\sqrt{WL}} \cdot \frac{i_G}{I}\right)^2$$

Outline

- **Scaling Effects**
- **Design Methodology**
- **Challenges in sub-28nm CMOS**
- **Analog Circuit Design for Sub-28nm CMOS**
- **Design Examples**
- **Conclusions**

Sub-28nm CMOS Circuit Design

 - Stack devices
 - Ensure no stressed oxides during off mode
 - Used in I/O drivers




Sub-28nm CMOS Circuit Design

- **Digitally assisted analog circuit design**
 - **Use trimming/calibration loops to sense imperfections in analog circuits → mismatches, center frequency, etc.**
 - **Data converters (DAC/ADC):**
 - **Use a higher resolution, lower frequency ADC/DAC to sense imperfections**
 - **Input voltage (or digital word) is a saw-tooth waveform during calibration**
 - **VCO:**
 - **Trim center frequency**
 - **Trim LC tank amplitude**

Sub-28nm CMOS Circuit Design

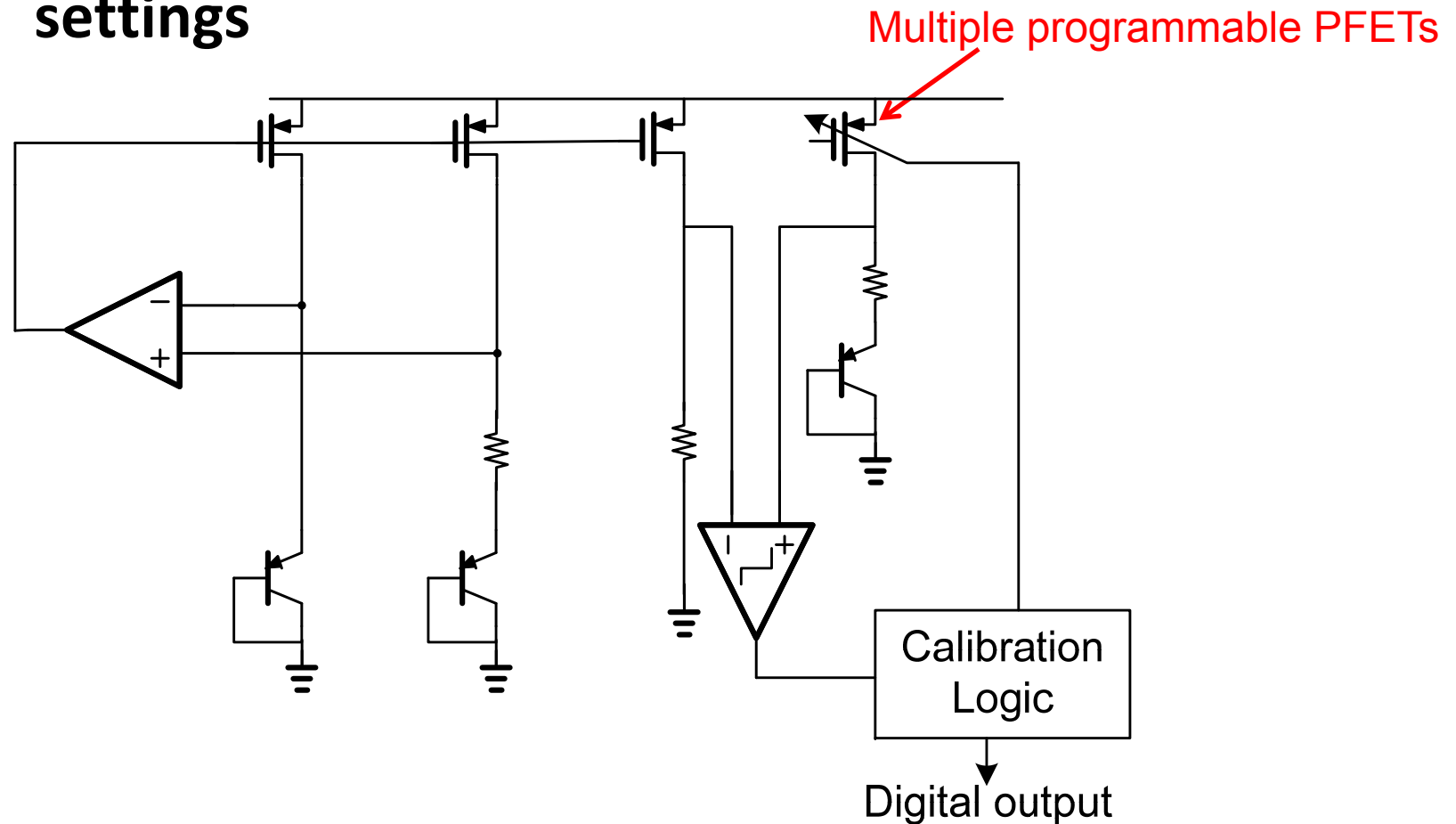- Design techniques:
 - Digital temperature sensor → use to adjust analog settings




Outline

- **Scaling Effects**
- **Design Methodology**
- **Challenges in sub-28nm CMOS**
- **Analog Design for Sub-28nm CMOS**
- **Design Examples**
- **Conclusions**

Design Examples

- 9-bit SAR ADC in 28nm CMOS

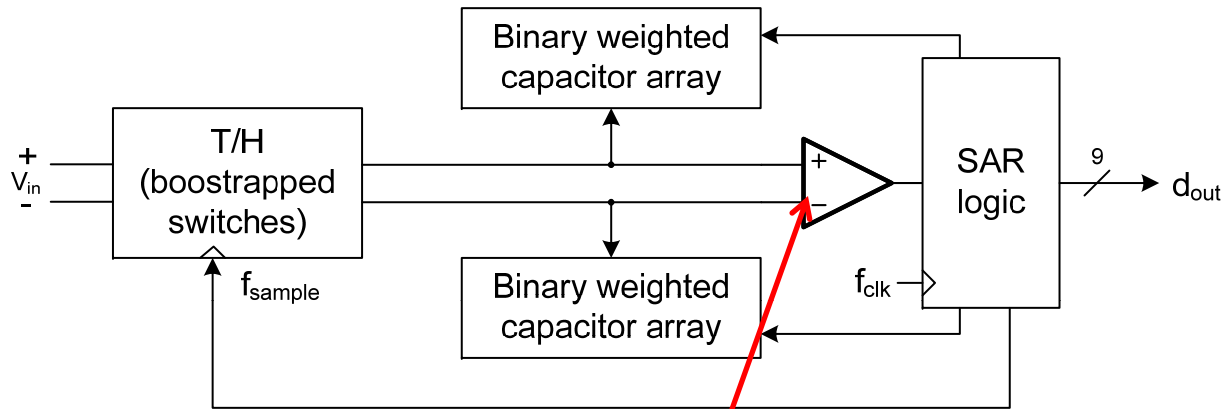


Input offset voltage
calibrated at startup
(DC calibration loop)

Performance Summary:


Metric	Value
# bits	9
V_{DD}	0.9
f_{CLK}	900MHz
Area	200um x 100um
Power	382uW
ENOB	8.51

Design Examples

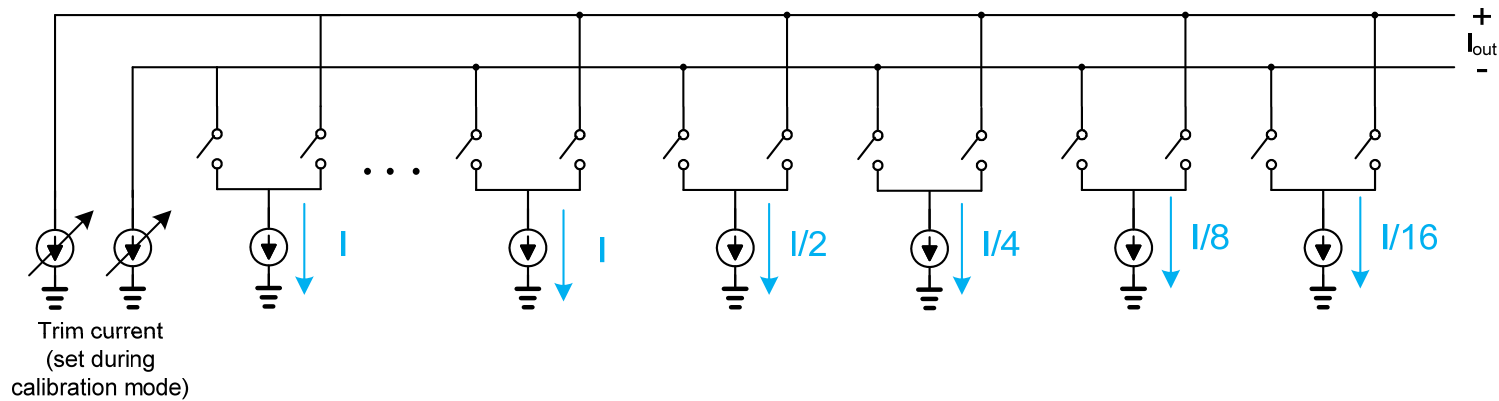- 10-bit current steering DAC in 28nm CMOS



- One Slice:

 


Performance Summary:

Metric	Value
# bits	10
V_{DD}	0.9
f_{CLK}	200MHz
Area	200um x 100um
Power	330uA
ENOB	8.8 bits

Design Examples

- VCO in 28nm CMOS:

PFET current mirror with embedded PSR

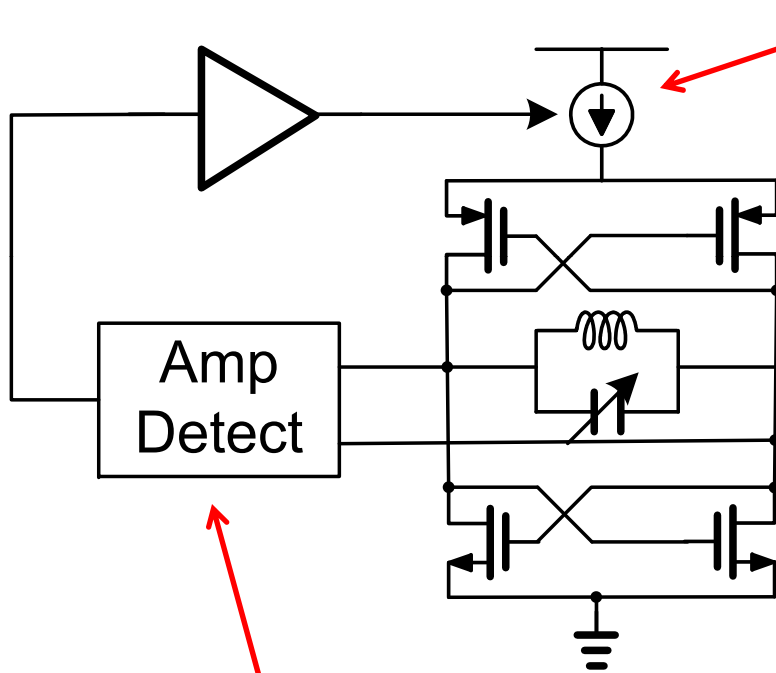

Current amplitude loop to suppress LO harmonics in LC tank.

Performance Summary:

Metric	Value
$F_{osc,center}$	3GHz
Tuning range	800MHz
PN @ 1MHz	-134.3dBc/Hz
Power	9mA

Outline

- **Scaling Effects**
- **Design Methodology**
- **Challenges in sub-28nm CMOS**
- **Analog Design for Sub-28nm CMOS**
- **Design Examples**
- **Conclusions**

Conclusions

- **Scaling Effects Reviewed**
- **Design Methodology**
 - **Based on gm/ID design methodology**
 - **Extended to include DR & BW**

Conclusions

- **Challenges in sub-28nm CMOS analog design**

DSM effect	Analog Circuit Implication
Stress effects (isolation proximity)	Mobility variation (BW, current mismatch, gain)
Diffusion proximity	VT variation (mismatch)
Gate leakage	Noise, mismatch, low-frequency limit

- **Analog circuit design techniques**

Design Technique	Reason / Application
FET stacking	High voltage swing
Digital assist / temp sensor	Trimming analog

- **Design examples: DAC, ADC, VCO**